

MOSFET

MOSFET Gate Drive Current Setting for Motor Application

Introduction

This document describes how to decide a gate drive current in motor application.

Gate driver and pre-driver which can be selected gate drive current are controlled sink and source current individually.

The gate drive current should be decided by and the required output switching time, peripheral parts, electrical characteristics of the MOSFET.

The document shows the behavior of MOSFET with in/out current flow on half-bridge topology driving. Then, gate drive current of high/low side is derived based on the required output switching time theoretically.

Application

All types of motor application with half-bridge topology. Three phase motor driving, H-bridge motor driving.

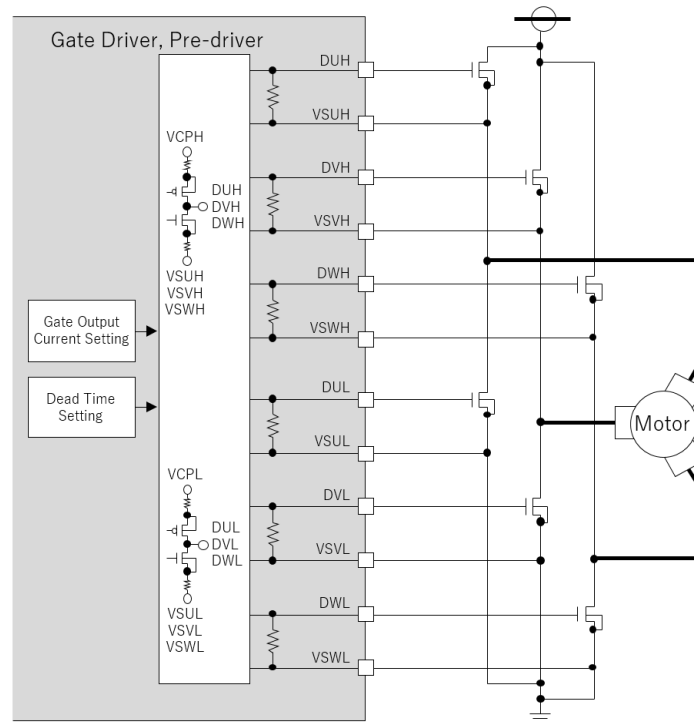


Figure 1. Motor application example:
Gate driver with constant-current gate drive for external MOSFET

Contents

Introduction	1
Application	1
Basic MOSFET operation in a half-bridge circuit when driving a motor	3
In case the MOSFET flows current into the motor coil by PWM operation	3
In case the MOSFET flows current out of the motor coil by PWM operation	3
Switching time and Transition time definition	4
Source current setting of low side MOSFET gate drive	6
Sink current setting of low side MOSFET gate drive	7
Output voltage transition when turned off does not become steeper than a certain point even if Isink is increased	8
Sink current setting of low side MOSFET drive to prevent self-turn-on	9
Source current setting of high side MOSFET gate drive	10
Sink current setting of high side MOSFET gate drive	11
Sink current setting of high side MOS-FET drive to prevent self-turn-on	12
Additional external capacitors to adjust transition time	12

Basic MOSFET operation in a half-bridge circuit when driving a motor

In case the MOSFET flows current into the motor coil by PWM operation

- ① High side MOSFET Q1 turns on.
Q1 supplies the motor current I_o .
The voltage at the output OUT rises to the supply voltage $V_M - R_{on} \cdot I_o$. Q1 continues to supply I_o .
- ② High side MOSFET Q1 turns off. To prevent shoot-through, there is a time to turn off the high side and low side MOSFETs at the same time.
Motor coil tries to keep I_o flowing.
OUT voltage falls and the motor current I_o continues to flow through the parasitic diode of the low side MOSFET Q2, which is turned off.
- ③ Low side MOSFET Q2 turns on. The motor current I_o flows through the turned-on Q2.
- ④ Low side MOSFET Q2 turns off.
To prevent shoot-through, there is a time to turn off the high side and low side MOSFETs at the same time.
Motor current I_o continues to flow through the parasitic diode of the low side MOSFET Q2
Operation returns to ①.

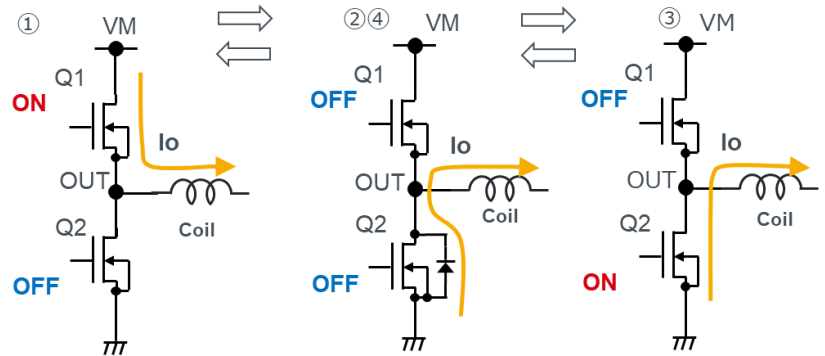


Figure 2. MOSFET operation of half-bridge circuit for coil drive during current into the motor coil.

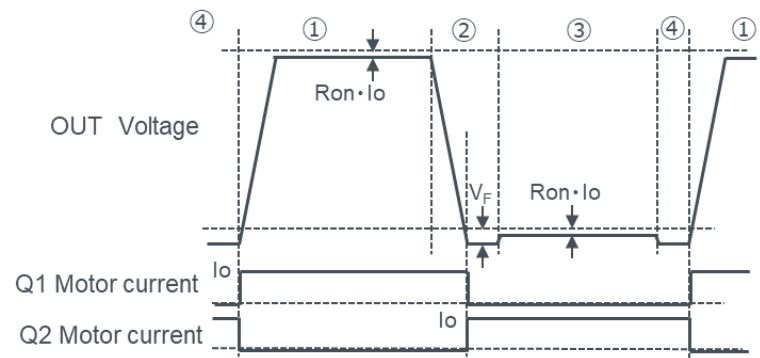


Figure 3. Half-bridge coil drive waveform during current into the motor coil.

In case the MOSFET flows current out of the motor coil by PWM operation

- ⑤ Low side MOSFET Q2 turns on.
Q2 supplies the motor current I_o .
The voltage at the output OUT falls to $R_{on} \cdot I_o$.
Q2 continues to supply I_o .
- ⑥ Low side MOSFET Q2 turns off. To prevent shoot-through, there is a time to turn off the high side and low side MOSFETs at the same time.
Motor coil tries to keep I_o flowing.
OUT voltage rises and the motor current I_o continues to flow through the parasitic diode of the high side MOSFET Q1, which is turned off.
- ⑦ High side MOSFET Q1 turns on. The motor current I_o flows through the turned-on Q1.

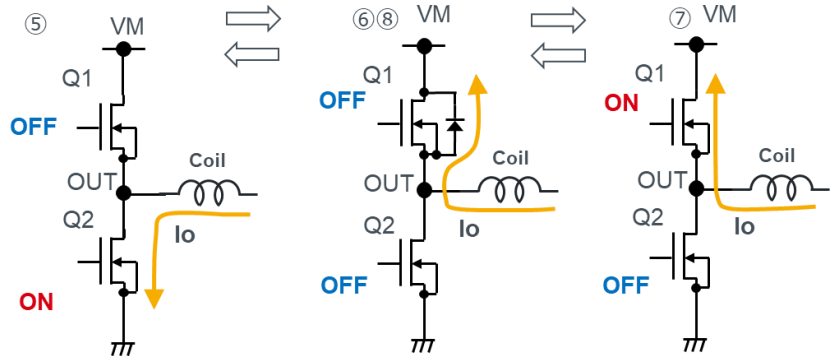


Figure 4. MOSFET operation of half-bridge circuit for coil drive during current out of the motor

⑧ High side MOSFET Q1 turns off.

To prevent shoot-through, there is a time to turn off the high side and low side MOSFETs at the same time.

Motor current I_o continues to flow through the parasitic diode of the high side MOSFET Q1

Operation returns to ⑤.

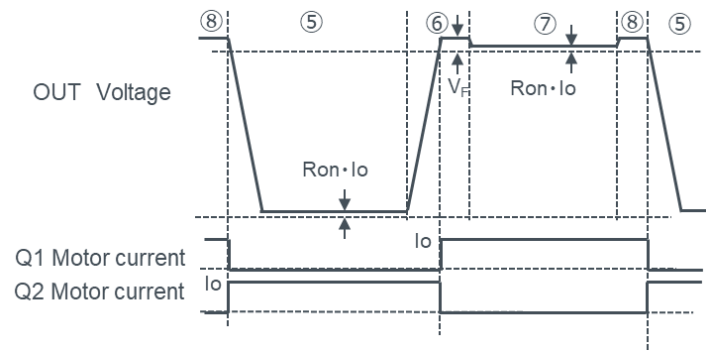


Figure 5. Half-bridge coil drive waveform during current out of the motor

Switching time and Transition time definition

Following time range should be decided based on your motor application.

- t_{sw} , t_{swOFF} : Switching time from the beginning of Gate voltage to the end of Output voltage transition

t_{sw} and t_{swOFF} affect to reduce the difference between duty ratio of input PWM from controller and duty ratio of output to the motor, and reduce acoustic noise by reducing the current distortion of three phase motors.

t_{swOFF} should be sufficient shorter than the dead time to prevent shoot-through.

- t_{ON} , t_{OFF} : Transition time for output voltage

t_{ON} and t_{OFF} are equivalent to slew rate of output. Slew rate affect to efficiency and EMC.

Source (outflow gate) current is decided by t_{sw} and t_{ON} . Sink (inflow gate) current is decided by t_{swOFF} and t_{OFF} .

Figure 6 shows timing chart of half-bridge for motor driving. Motor pre-driver or gate driver outputs gate current control signal with dead time.

Detailed behavior of No.1 to No.35 is as follows:

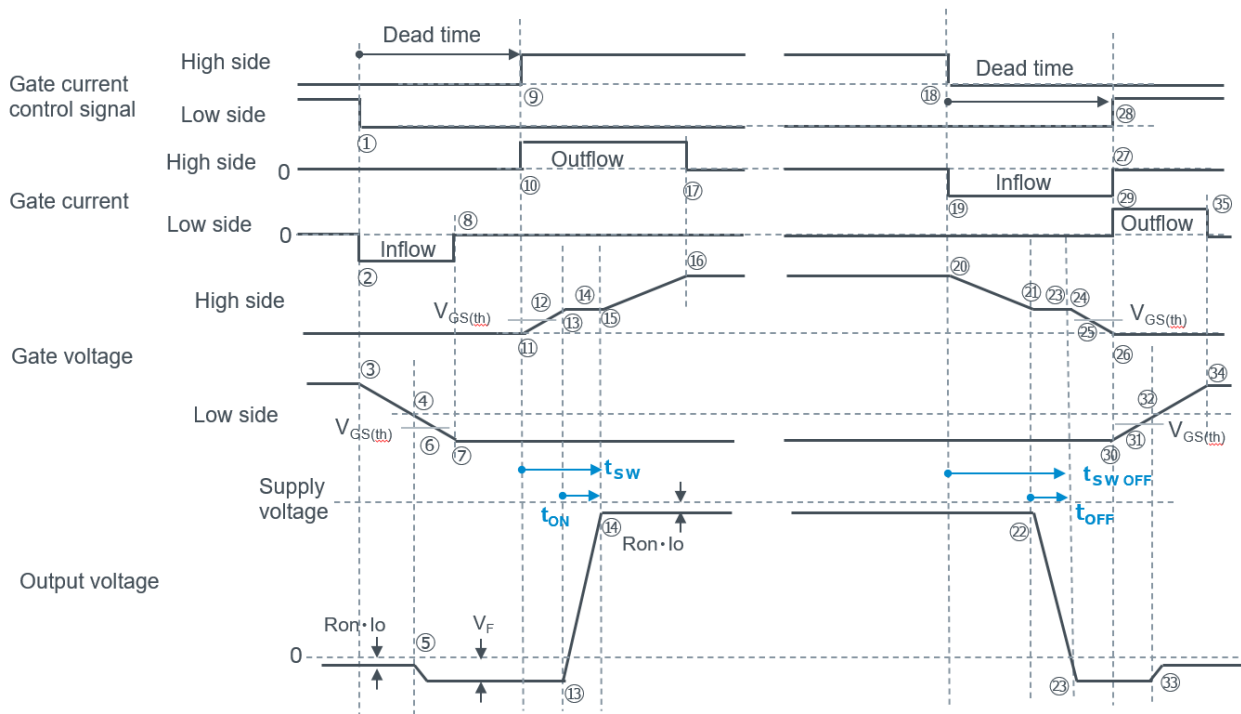


Figure 6. Timing chart for Half-bridge on motor drive application [Motor current out]



Source current setting of low side MOSFET gate drive

This parameter affects to the low side Nch MOSFET is on.

The source current value (I_{source}) can be calculated by deciding either following value on your demand. (See p.4 and Fig. 8,9):

- (1) t_{ON} : Transition time for output voltage (V_{DS})
- (2) t_{SW} : Switching time from the beginning of V_{GS} to the end of V_{DS} transition.

(1) Calculate low side source current with t_{ON}

Source current I_{source} is calculated by the electrical charge Q_{gd} and the time t_{ON} .

$$I_{source} = \frac{Q_{gd}}{t_{ON}} \quad (1)$$

Q_{gd} : the required electrical charge from high to low of V_{DS} .

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V, I_D=40A$)

- Specification (Tentative):

$Q_{gd}=2.0nC$ (typ)(conditions: $V_{DD}\approx 20V, I_D=10A, V_{GS}=6V$)

- User Required: (Applicable value for motor application)

$t_{ON}=200ns$

Required low side source current is:

$$I_{source} = \frac{2.0nC}{200ns} = 20mA \quad (2)$$

(2) Calculate low side source current with t_{SW}

Source current I_{source} is calculated by the electrical charge Q_{gd} , Q_{gs} and the time t_{SW} .

$$I_{source} = \frac{Q_{gs}+Q_{gd}}{t_{SW}} \quad (3)$$

Q_{gd} : the required electrical charge from high to low of V_{DS} .

Q_{gs} : the required electrical charge from zero to flat of V_{GS} .

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V, I_D=40A$)

- Specification (Tentative):

$Q_{gs}=1.2nC$ (typ), $Q_{gd}=2.0nC$ (typ)(conditions: $V_{DD}\approx 20V, I_D=10A, V_{GS}=4.5V$)

- User Required: (Applicable value for motor application)

$t_{SW}=500ns$ (1/100 for general PWM frequency 20 kHz)

Required low side source current is:

$$I_{source} = \frac{1.2nC+2.0nC}{500ns} = 6.4mA \quad (4)$$

However, since Q_{gs} and Q_{gd} change with the voltage and current used, correction is necessary in such cases.

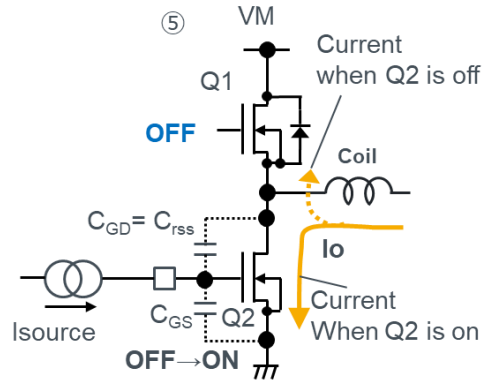


Figure 7. Equivalent circuit at low side on

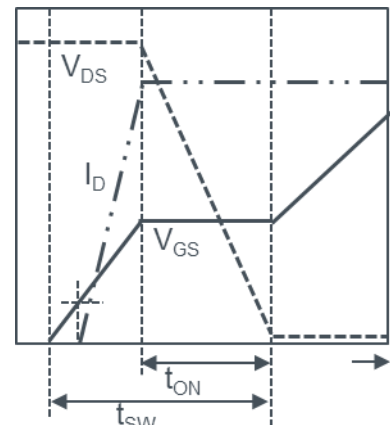


Figure 8. Switching transient waveform

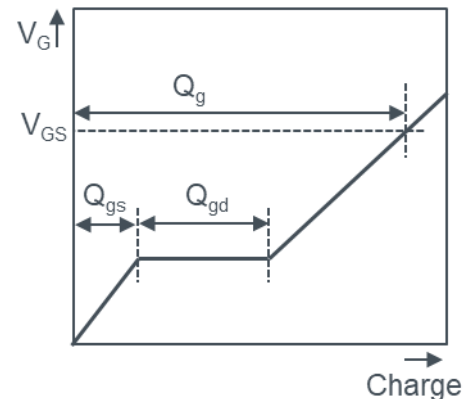


Figure 9. Gate voltage vs. gate charge characteristics

Sink current setting of low side MOSFET gate drive

This parameter affects to the low side Nch MOSFET is off.
 The sink current value (I_{sink}) can be calculated by deciding either following value on your demand. (See p.4 and Fig.11,12):

- (3) $t_{SW OFF}$: Switching time from the beginning of V_{GS} to the end of V_{DS} transition.
- (4) t_{OFF} : Transition time for output voltage

(3) Calculate low side sink current with $t_{SW OFF}$

Electrical charge Q_{GS2} calculated by the voltage V_{GSDL} , V_{PLT} and the capacitance C_{iss} .

$$Q_{GS2} = (V_{GSDL} - V_{PLT}) \times C_{iss} \quad (5)$$

- Q_{GS2} : the required electrical charge from maximum to flat of V_{GS} .
- V_{GSDL} : the maximum voltage of the output circuit that drives the gate.
- V_{PLT} : the flat voltage when the gate voltage changes.
- C_{iss} : input capacitance of MOSFET

Sink current I_{sink} is calculated by the electrical charge Q_{GS2} , Q_{gs} and the time $t_{SW OFF}$.

$$I_{sink} = (Q_{GS2} + Q_{gd}) / t_{SW OFF} = \{(V_{GSDL} - V_{PLT}) \times C_{iss} + Q_{gd}\} / t_{SW OFF} \quad (6)$$

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V, I_D=40A$)

- Specification (Tentative):

$C_{iss}=700pF$ (typ) (conditions: $V_{DS}\approx 20V, V_{GS}=0V, f=1MHz$)

$Q_{gd}=2.0nC$ (typ) (conditions: $V_{DD}\approx 20V, I_D=10A, V_{GS}=6V$)

$V_{PLT}=2.1V$ (typ) (conditions: $V_{DD}\approx 20V, I_D=10A, V_{GS}=10V$)

ROHM Three phase sensor-less motor pre-driver

- Specification (Tentative):

$V_{GSDL}=9.5V$ (typ) (conditions: $V_{CC} = 5.5V$ to $18V, I_O=-20mA$ at $I_{SOURCE}=-31mA$ setting)

- User Required: (Applicable value for motor application)

$t_{SW}=500ns$ (1/100 for general PWM frequency 20 kHz)

Required low side sink current is:

$$I_{sink} = \{(9.5V - 2.1V) \times 700pF + 2.0nC\} / 500ns = (5.18nC + 2.0nC) / 500nC = 14.4mA \quad (7)$$

(4) Calculate low side sink current with t_{OFF}

Sink current I_{sink} is calculated by the electrical charge Q_{gd} and the time t_{OFF} .

$$I_{sink} = Q_{gd} / t_{OFF} \quad (8)$$

Q_{gd} : the required electrical charge from low to high of V_{DS} .

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V, I_D=40A$)

- Specification (Tentative):

$Q_{gd}=2.0nC$ (typ) (conditions: $V_{DD} \approx 20V, I_D=10A, V_{GS}=6V$)

- User Required: (Applicable value for motor application)

$t_{ON}=200ns$

Required low side sink current is:

$$I_{sink} = 2.0nC / 200ns = 10.0mA \quad (9)$$

Recalculated t_{OFF} by 14.4mA of equation (7) is:

$$t_{OFF} = Q_{gd} / I_{sink} = 2.0nC / 14.4mA = 139ns \quad (10)$$

Confirm that there is no ringing in the output waveform.

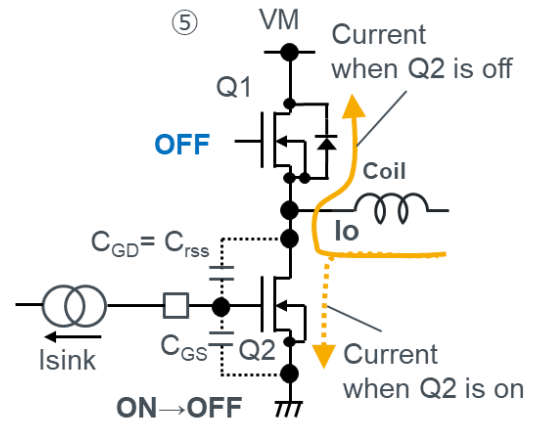


Figure 10. Equivalent circuit at low side off

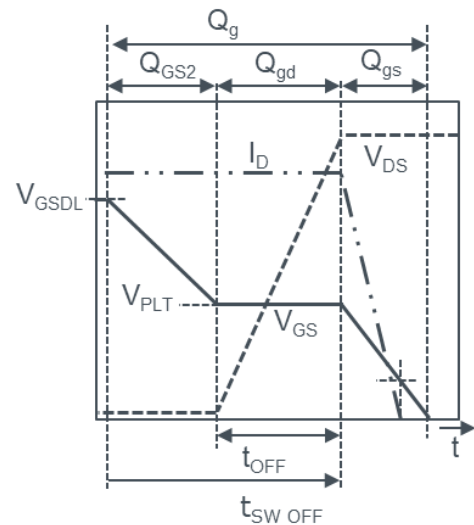


Figure 11. Switching transient waveform

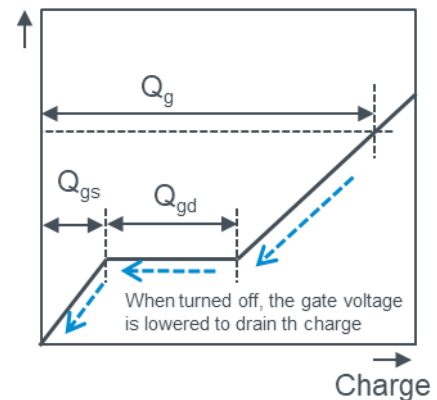


Figure 12. Gate voltage vs. gate charge characteristics

Output voltage transition when turned off does not become steeper than a certain point even if Isink is increased.

When current is applied to the motor coil by PWM drive, the coil part can be regarded as a constant current load. When Q2 is turned off and the output voltage rises by constant current, the capacitor connected to the Q2 drain is charged to change the voltage. Output current I_o charges C_{oss} of high side and low side MOSFET and output-to-GND capacitor C_{out} for noise rejection. the output voltage transition dV_{DS}/dt is as follows.

$$dV_{DS}/dt = I_o / (C_{oss(Q1)} + C_{oss(Q2)} + C_{out}) \quad (11)$$

Output voltage transitions cannot be greater than this, even if gate sink current increases.

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification (Tentative):

$C_{oss}=900pF$ (conditions: $V_{DS}=0V$, $V_{GS}=0V$, $f=1MHz$)

$C_{oss}=430pF$ (conditions: $V_{DS}=12V$, $V_{GS}=0V$, $f=1MHz$)

- Output-to-GND capacitor

$C_{out}=0nF$

- Output current

$I_o=5A$

- Supply voltage

$VM=12v$

Output voltage transition is:

$$dV_{DS}/dt = 5A / (0.90nF + 0.43nF + 0nF) = 3.76V/ns \quad (12)$$

Output transition time is:

$$t_{OFF} = VM / (dV_{DS}/dt) = 12V / 3.76V/ns = 3.19ns \quad (13)$$

Output voltage transition when turned off is The later of the value determined by output current and output capacitor or the value determined by gate sink current and C_{rss} .

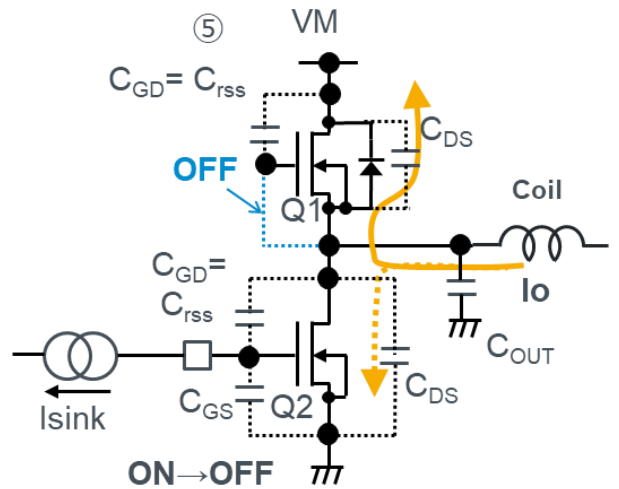


Figure 13. Equivalent circuit 2 at low side off

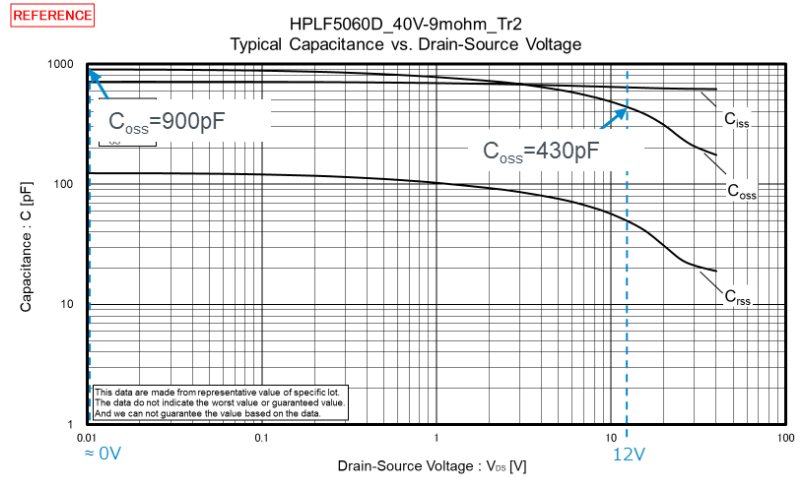


Figure 14. MOSFET Capacitance vs. Drain- Source voltage characteristic

Sink current setting of low side MOSFET drive to prevent self-turn-on

To prevent self-turn-on, changes in drain-source voltage must be such that the current charging the gate-drain capacitor $C_{r_{ss}}$ raises the gate-source voltage and does not exceed the gate threshold voltage.

If the change in drain-source voltage is dV_{DS}/dt , the current $I_{C_{r_{ss}}-C_{G_S}}$ flowing from $C_{r_{ss}}$ through C_{G_S} is:

$$I_{C_{r_{ss}}-C_{G_S}} = (C_{r_{ss}} \times C_{G_S}) / (C_{r_{ss}} + C_{G_S}) \times dV_{DS}/dt \quad (14)$$

If the gate current I_{sink} is flowed out of the connection point between $C_{r_{ss}}$ and C_{G_S} , the current $I_{C_{G_S}}$ flowing into C_{G_S} is:

$$I_{C_{G_S}} = I_{C_{r_{ss}}-C_{G_S}} - I_{sink} = (C_{r_{ss}} \times C_{G_S}) / (C_{r_{ss}} + C_{G_S}) \times dV_{DS}/dt - I_{sink} \quad (15)$$

Approximating that V_{DS} varies from 0V to the supply voltage V_M during time t_1 , dV_{DS}/dt is:

$$dV_{DS}/dt = V_M/t_1 \quad (16)$$

The voltage $V_{C_{G_S}}$ generated at C_{G_S} is:

$$V_{C_{G_S}} = \frac{1}{C_{G_S}} \int_0^{t_1} I_{C_{G_S}} dt = \frac{1}{C_{G_S}} \int_0^{t_1} \left(\frac{C_{r_{ss}} \times C_{G_S}}{C_{r_{ss}} + C_{G_S}} \times \frac{V_M}{t_1} - I_{sink} \right) dt = \frac{C_{r_{ss}}}{C_{r_{ss}} + C_{G_S}} \times V_M - \frac{1}{C_{G_S}} \times I_{sink} \times t_1 \quad (17)$$

Because Q2 is not turned on when $V_{C_{G_S}}$ is less than V_{th} of Q2,

$$V_{th} \geq \frac{C_{r_{ss}}}{C_{r_{ss}} + C_{G_S}} \times V_M - \frac{1}{C_{G_S}} \times I_{sink} \times t_1 \quad (18)$$

$$I_{sink} \geq \left(\frac{C_{r_{ss}}}{C_{r_{ss}} + C_{G_S}} \times V_M - V_{th} \right) \times \frac{C_{G_S}}{t_1} \quad (19)$$

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification(Tentative):

$C_{iss}=700pF$, $C_{r_{ss}}=120pF$ (conditions: $V_{DD} \approx 0V$, $V_{GS}=0V$, $f=1MHz$)

$C_{GS} = C_{iss} - C_{r_{ss}} = 580pF$

$V_{GS(th)} = 2.0V(\text{min})$ (conditions: $V_{DS}=V_{GS}$, $I_D=1mA$)

Assuming 0.63V drop at $T_j=150^\circ C$ due to temperature characteristics,

$V_{GS(th)}=1.37V(\text{Min})$

-The supply voltage

$V_M=12V$.

- t_1 is the time to the point where the tangent line of the steepest point of V_{DS} and the supply voltage intersect in actual operation. Set t_1 to 1/2 of t_{ON} . (See Fig.16)

$t_1=100ns$

$$\begin{aligned} I_{sink} &\geq \left(\frac{120pF}{700pF} \times 12V - 1.37V \right) \times \frac{580pF}{100ns} \\ &= (2.06V - 1.37V) \times \frac{580pF}{100ns} \\ &= 4.0mA \quad (20) \end{aligned}$$

If sink=10mA, $V_{C_{G_S}}$ is:

$$\begin{aligned} V_{C_{G_S}} &= \frac{120pF}{700pF} \times 12V - \frac{1}{580pF} \times 10mA \times 100ns \\ &= 2.06V - 1.72V \\ &= 0.34V \quad (21) \end{aligned}$$

Because $V_{C_{G_S}}$ is under $V_{GS(th)}$ [1.37V(min) (at $T_j=150^\circ C$)], Self-turn-on does not occur.

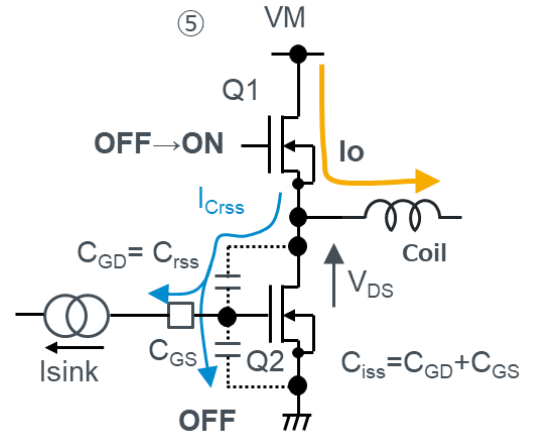


Figure 15. Equivalent circuit at self-turn-on

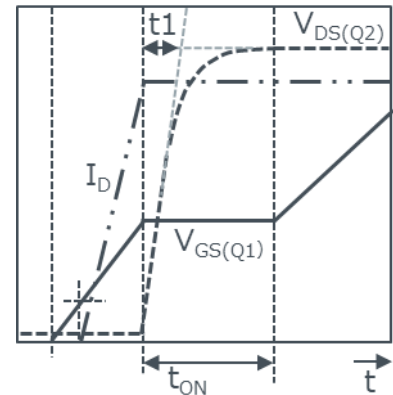


Figure 16. Q2 V_{DS} actual waveform when Q1 is on

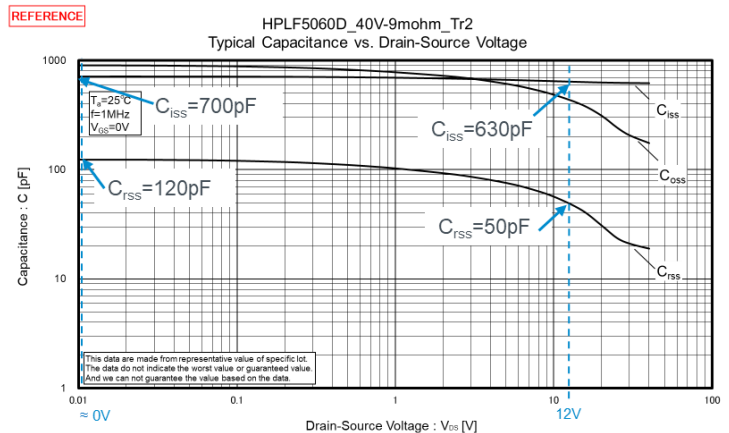


Figure 17. MOSFET capacitance - Drain-source voltage characteristics

Source current setting of high side MOSFET gate drive

When current flows into the gate of the high side Nch MOSFET, the gate voltage rises and reaches V_{GS} , which allows the motor current to flow, the source voltage V_s of Q1 rises, and the gate voltage V_G rises with it.

The drain voltage V_D is constant. For this reason, the relative gate-source voltage V_{GS} and the drain-source voltage V_{DS} are similar to the operation of the low side MOS-FET.

This parameter affects to the high side Nch MOS-FET is on. The source current value (I_{source}) can be calculated by deciding either following value on your demand. (See p.4 and Fig. 20):
 (1) t_{ON} : Transition time for output voltage
 (2) t_{sw} : Switching time from the beginning of V_{GS} to the end of V_{DS} transition.

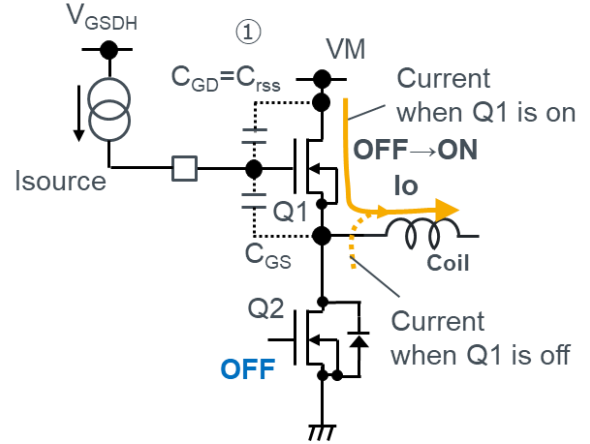


Figure 18. Equivalent circuit at high side on

(1) Calculate low high source current with t_{ON}

Source current I_{source} is calculated by the required electrical charge Q_{gd} and the time t_{ON} .

$$I_{source} = \frac{Q_{gd}}{t_{ON}} \quad (22)$$

Q_{gd} : the required electrical charge from high to low of V_{DS} .

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification (Tentative):

$Q_{gd}=2.0nC$ (typ)(conditions: $V_{DD}\approx 20V$, $I_D=10A$, $V_{GS}=6V$)

- User Required: (Applicable value for motor application)

$t_{ON}=200ns$

Required low side source current is:

$$I_{source} = \frac{2.0nC}{200ns} = 20mA \quad (23)$$

(2) Calculate high side source current with t_{sw}

Source current I_{source} is calculated by the required electrical charge Q_{gd} , Q_{gs} and the time t_{sw} .

$$I_{source} = \frac{Q_{gs} + Q_{gd}}{t_{sw}} \quad (24)$$

Q_{gd} : the required electrical charge from high to low of V_{DS} .

Q_{gs} : the required electrical charge from zero to flat of V_{GS} .

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification (Tentative):

$Q_{gs}=1.2nC$ (typ), $Q_{gd}=2.0nC$ (typ)(conditions: $V_{DD}\approx 20V$, $I_D=10A$, $V_{GS}=4.5V$)

- User Required: (Applicable value for motor application)

$t_{sw}=500ns$ (1/100 for general PWM frequency 20 kHz)

Required low side source current is:

$$I_{source} = \frac{1.2nC + 2.0nC}{500ns} = 6.4mA \quad (25)$$

However, since Q_{gs} and Q_{gd} change with the voltage and current used, correction is necessary in such cases.

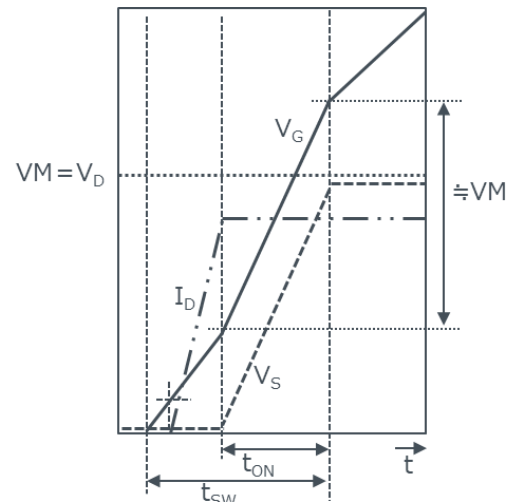


Figure 19. Switching transient waveform (Absolute value)

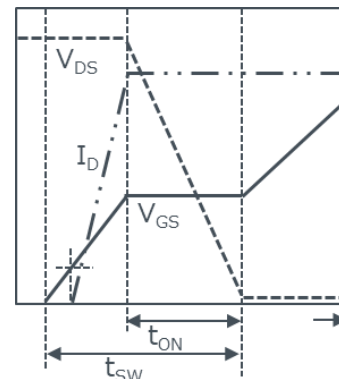


Figure 20. Switching transient waveform (Relative value)

Sink current setting of high side MOSFET gate drive

The operation from full on to off is the same as the operation of the low side MOS-FET.

This parameter affects to the high side Nch MOSFET is off. The sink current value (I_{sink}) can be calculated by deciding either following value on your demand. (See p.4 and Fig.23) :

- (3) $t_{SW OFF}$: Switching time from the beginning of V_{GS} to the end of V_{DS} transition.
- (4) t_{OFF} : Transition time for output voltage

(3) Calculate high side sink current with $t_{SW OFF}$

Electrical charge Q_{GS2} is calculated by the voltage V_{GSDL} , V_{PLT} and the capacitance C_{iss} .

$$Q_{GS2} = (V_{GSDL} - VM - V_{PLT}) \times C_{iss} \quad (26)$$

- Q_{GS2} : the required electrical charge from maximum to flat of V_{GS} .
- V_{GSDL} : the maximum voltage of the output circuit that drives the gate.
- VM : power supply voltage
- V_{PLT} : the flat voltage when the gate voltage changes.
- C_{iss} : input capacitance of MOS-FET

Sink current I_{sink} is calculated by the required electrical charge Q_g , Q_{gs} and the time $t_{SW OFF}$.

$$I_{sink} = (Q_{GS2} + Q_{gd}) / t_{SW OFF} = \{ (V_{GSDL} - V_{PLT}) \times C_{iss} + Q_{gd} \} / t_{SW OFF} \quad (27)$$

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification (Tentative):
- $C_{iss}=700pF$ (typ) (conditions: $V_{DS}\approx 20V$, $V_{GS}=0V$, $f=1MHz$)
- $Q_{gd}=2.0nC$ (typ) (conditions: $V_{DD}\approx 20V$, $I_D=10A$, $V_{GS}=6V$)
- $V_{PLT}=2.1V$ (typ) (conditions: $V_{DD}\approx 20V$, $I_D=10A$, $V_{GS}=10V$)

ROHM Three phase sensor-less motor pre-driver

- Specification (Tentative):
- $V_{GSDL}=VM+9.5V$ (typ) (conditions: $VM = 5.5V$ to $18V$, $I_O=-20mA$ at $I_{SOURCE}=-31mA$ setting)
- User Required: (Applicable value for motor application)
- $t_{SW}=500ns$ (1/100 for general PWM frequency 20 kHz)

Required low side sink current is:

$$I_{sink} = \{ (9.5V - 2.1V) \times 700pF + 2.0nC \} / 500ns = (5.18nC + 2.0nC) / 500nC = 14.4mA \quad (28)$$

(4) Calculate low side sink current with t_{OFF}

Sink current I_{sink} is calculated by the required electrical charge and the time t_{OFF} .

Q_{gd} is determined as the required electrical charge from low to high of V_{DS} .

$$I_{sink} = Q_{gd} / t_{OFF} \quad (29)$$

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{DSS}=40V$, $I_D=40A$)

- Specification (Tentative):
- $Q_{gd}=2.0nC$ (typ) (conditions: $V_{DD}\approx 20V$, $I_D=10A$, $V_{GS}=6V$)
- User Required: (Applicable value for motor application)
- $t_{ON}=200ns$

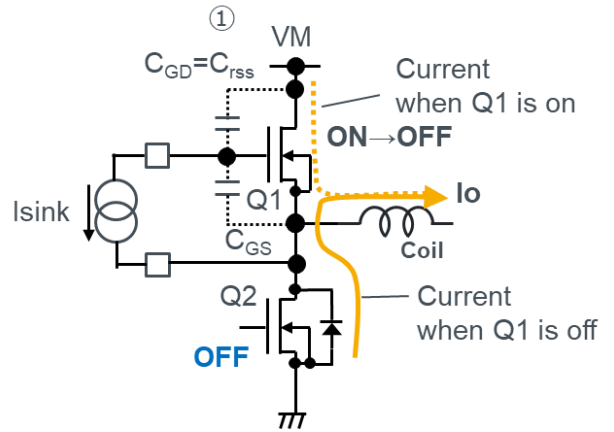


Figure 21. Equivalent circuit at high side off

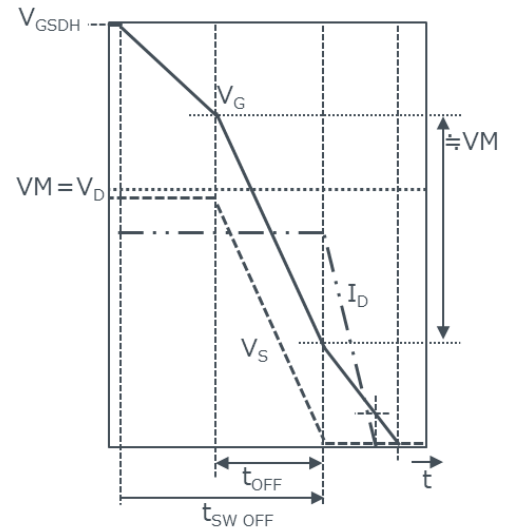


Figure 22. Switching transient waveform (Absolute value)

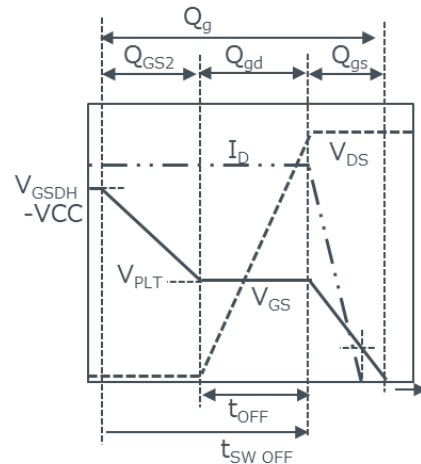


Figure 23. Switching transient waveform (Relative value)

Required low side sink current is:

$$I_{\text{sink}} = 2.0\text{nC}/200\text{ns} = 10.0\text{mA} \quad (30)$$

Recalculated t_{OFF} by 14.4mA of equation (28) is:

$$t_{\text{OFF}} = Q_{\text{gd}}/I_{\text{sink}} = 2.0\text{nC}/14.4\text{mA} = 139\text{ns} \quad (31)$$

Confirm that there is no ringing in the output waveform.

Sink current setting of high side MOS-FET drive to prevent self-turn-on

Even in the case where the high side MOSFET is turned off, when the low side MOSFET is turned on, the gate voltage of the high side MOSFET falls steeply. Since the drain of the high side MOSFET is constant by the supply voltage V_M , current flows through the gate-to-drain capacitor C_{rds} . To prevent self-turn-on, the gate-source voltage of high side MOSFET must be prevented from rising above the gate threshold voltage by C_{rds} current. Set the sink current using the same approach as for the low side MOSFET. (See Page 9.)

Additional external capacitors to adjust transition time

An external capacitor between gate and drain may use for adjusting switching and transition time (C_{GDEX} of Fig.24).

t_{ON} (Output voltage transient time) of low side MOSFET with external capacitor is as follows:

$$t_{\text{ON}} = (V_M \times C_{\text{GDEX}} + Q_{\text{gd}}) / I_{\text{source}} \quad (32)$$

t_{ON} : Output voltage transition time from $V_M[V]$ to 0V.

C_{GDEX} : Capacitance of external capacitor

Q_{gd} : Required electrical charge from high to low of V_{DS}

I_{source} : Supply current from driver to gate of MOSFET

t_{ON} of high side MOSFET with external capacitor is as the same.

[Example]

ROHM Nch Dual MOSFET (HPLF5060, $V_{\text{DSS}}=40\text{V}$, $I_{\text{D}}=40\text{A}$)

- Specification (Tentative):

$Q_{\text{gd}}=2.0\text{nC}$ (typ) (conditions: $V_{\text{DD}} \approx 20\text{V}$, $I_{\text{D}}=10\text{A}$, $V_{\text{GS}}=6\text{V}$)

-Supply voltage

$V_M=12\text{V}$

-External capacitor between Gate and Drain

$C_{\text{GDEX}}=330\text{pF}$

-Source current setting (Using previous setting, see page 6)

$I_{\text{source}}=10\text{mA}$

Output voltage transient time is:

$$t_{\text{ON}} = (12\text{V} \times 330\text{pF} + 2.0\text{nC})/10\text{mA}=596\text{ns} \quad (33)$$

t_{ON} is (596ns-200ns =) 396ns slower than the first value.

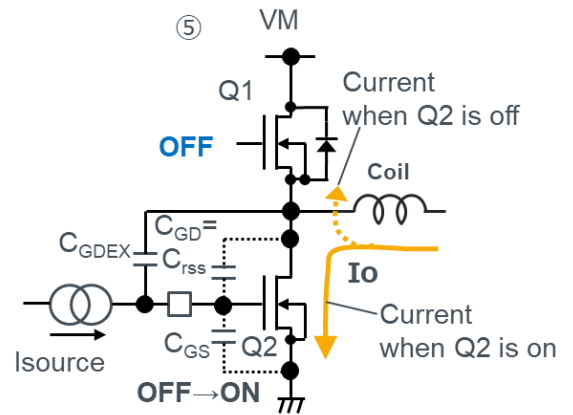


Figure 24. Equivalent circuit with external capacitor added between low side MOSFET gate and drain

Notice

- 1) The information contained in this document is intended to introduce ROHM Group (hereafter referred to as ROHM) products. When using ROHM products, please verify the latest specifications or datasheets before use.
- 2) ROHM products are designed and manufactured for use in general electronic equipment and applications (such as Audio Visual equipment, Office Automation equipment, telecommunication equipment, home appliances, amusement devices, etc.) or specified in the datasheets. Therefore, please contact the ROHM sales representative before using ROHM products in equipment or devices requiring extremely high reliability and whose failure or malfunction may cause danger or injury to human life or body or other serious damage (such as medical equipment, transportation, traffic, aircraft, spacecraft, nuclear power controllers, fuel control, automotive equipment including car accessories, etc. hereafter referred to as Specific Applications). Unless otherwise agreed in writing by ROHM in advance, ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of ROHM Products for Specific Applications.
- 3) Electronic components, including semiconductors, can fail or malfunction at a certain rate. Please be sure to implement, at your own responsibilities, adequate safety measures including but not limited to fail-safe design against physical injury, and damage to any property, which a failure or malfunction of products may cause.
- 4) The information contained in this document, including application circuit examples and their constants, is intended to explain the standard operation and usage of ROHM products, and is not intended to guarantee, either explicitly or implicitly, the operation of the product in the actual equipment it will be used. As a result, you are solely responsible for it, and you must exercise your own independent verification and judgment in the use of such information contained in this document. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of such information.
- 5) When exporting ROHM products or technologies described in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, such as the Foreign Exchange and Foreign Trade Act and the US Export Administration Regulations, and follow the necessary procedures in accordance with these provisions.
- 6) The technical information and data described in this document, including typical application circuits, are examples only and are not intended to guarantee to be free from infringement of third parties intellectual property or other rights. ROHM does not grant any license, express or implied, to implement, use, or exploit any intellectual property or other rights owned or controlled by ROHM or any third parties with respect to the information contained herein.
- 7) No part of this document may be reprinted or reproduced in any form by any means without the prior written consent of ROHM.
- 8) All information contained in this document is current as of the date of publication and subject to change without notice. Before purchasing or using ROHM products, please confirm the latest information with the ROHM sales representative.
- 9) ROHM does not warrant that the information contained herein is error-free. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties resulting from errors contained in this document.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<https://www.rohm.com/contactus>