
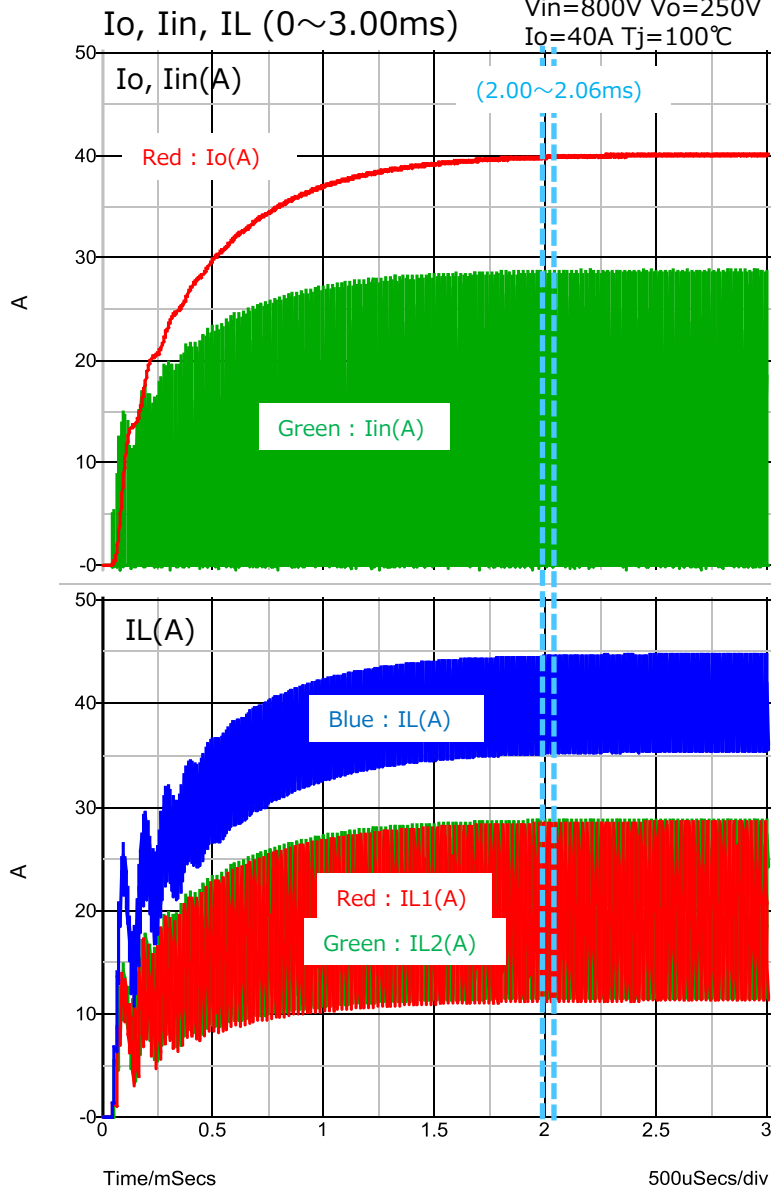


Simulation Waveform 1

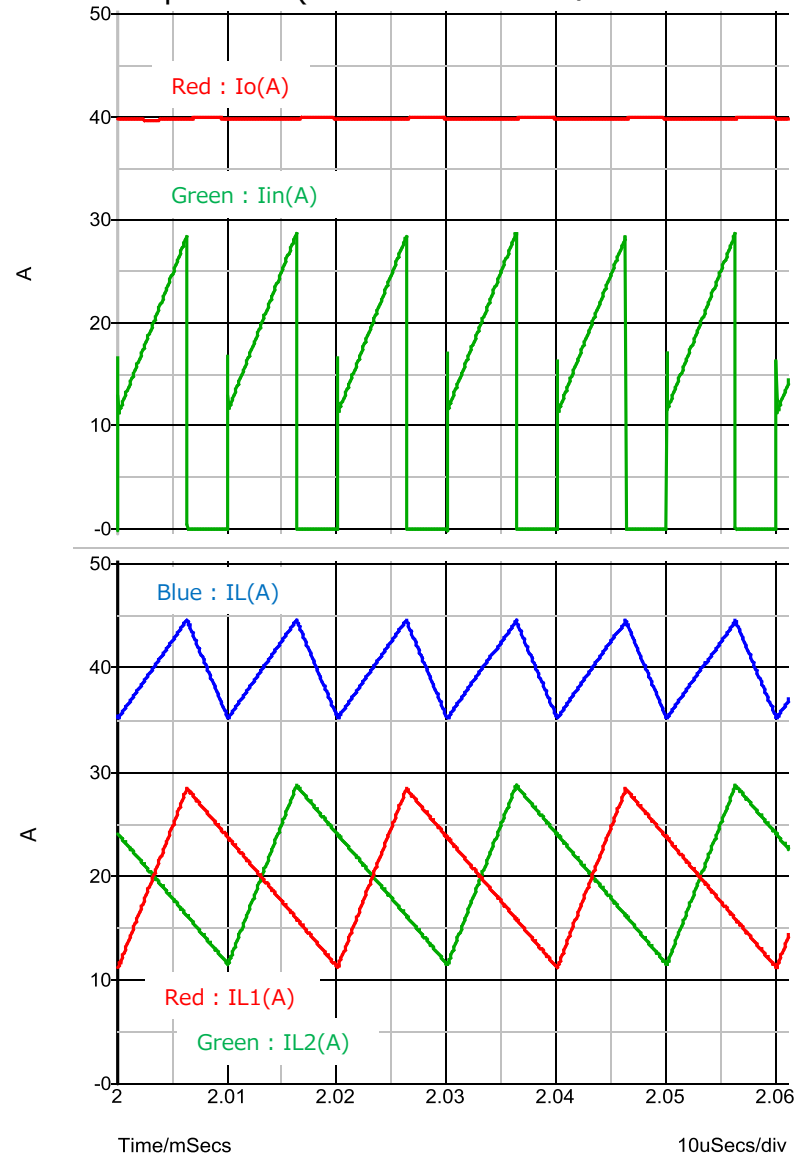$V_{in}=800V$ $V_o=250V$
 $I_o=40A$ $T_j=100^{\circ}C$




Expansion (2.00ms~2.06ms)




Simulation Waveform 2





Vin=800V Vo=250V
Io=40A Tj=100°C

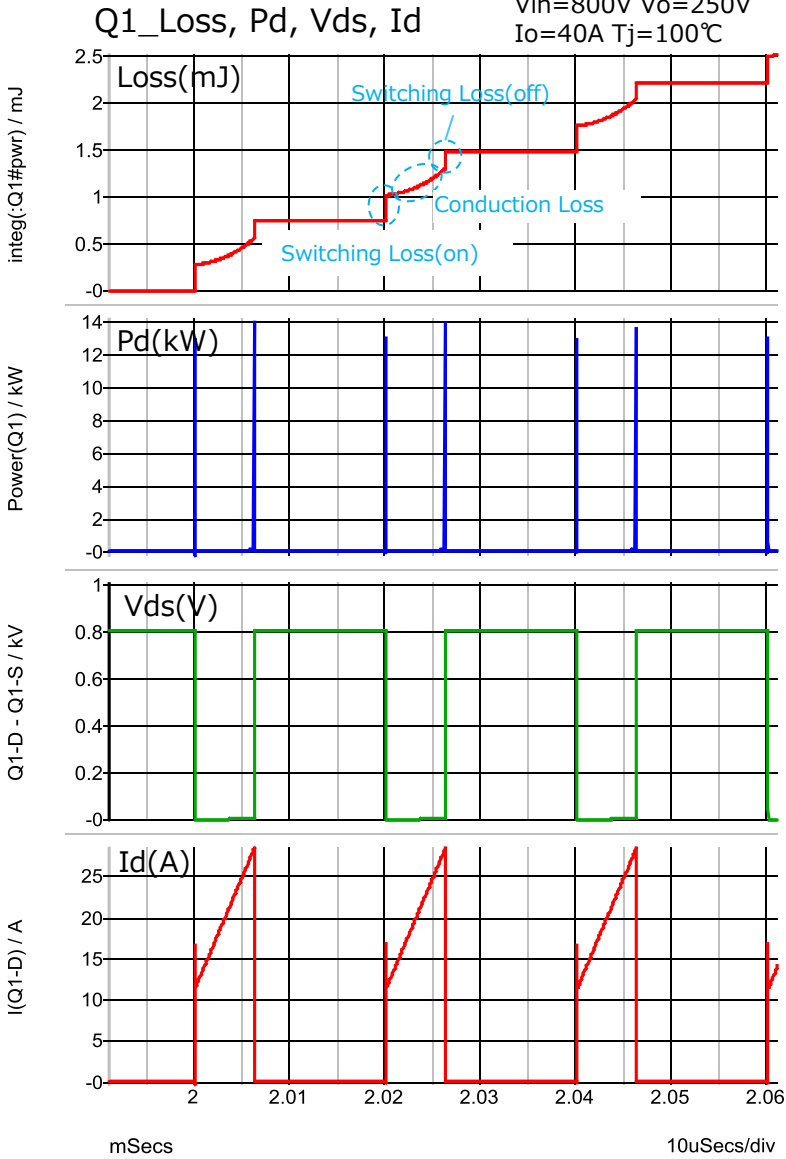

Vin=800V Vo=250V
Io=40A Tj=100°C

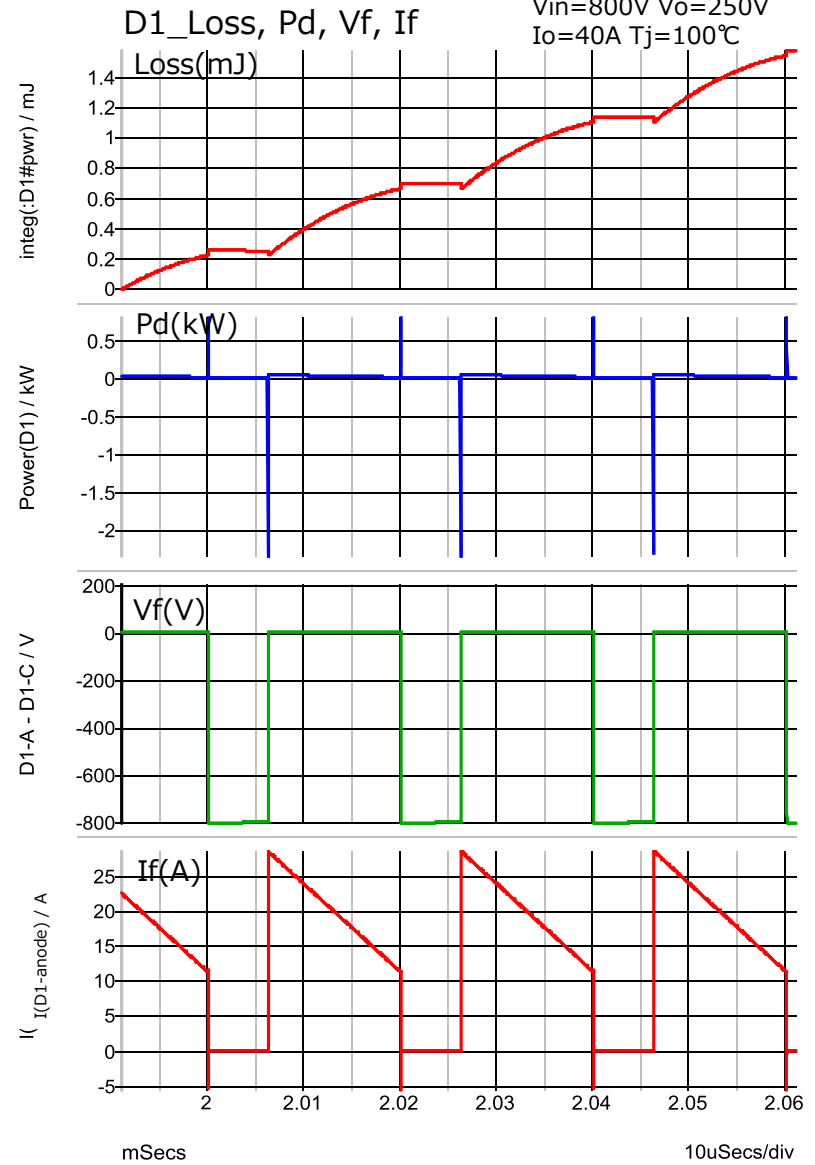

Efficiency, Power Dissipation 1

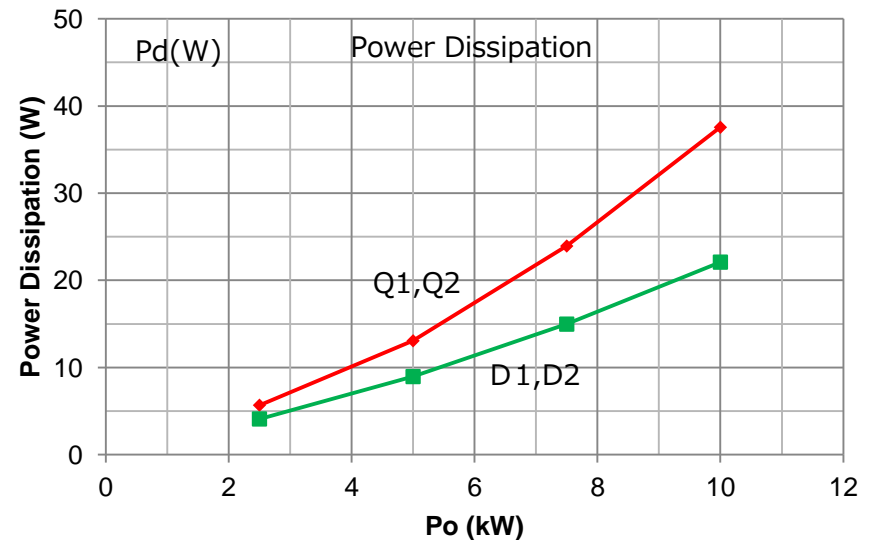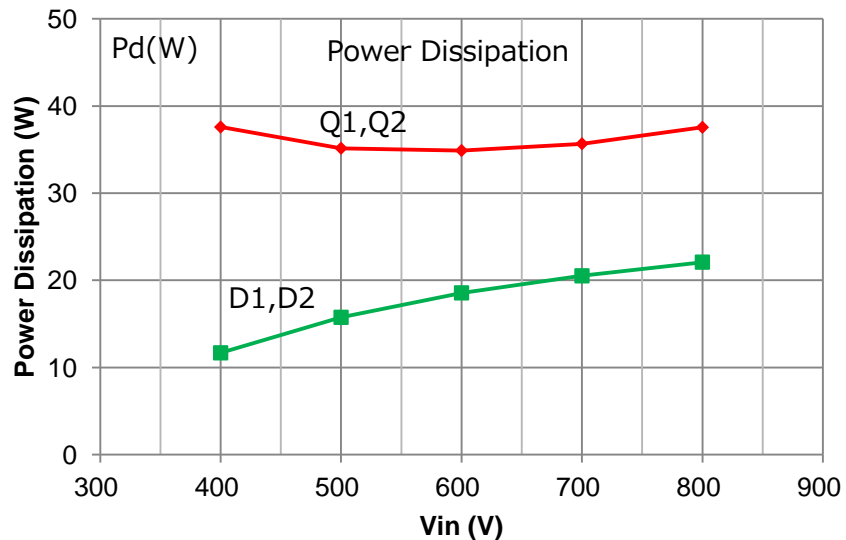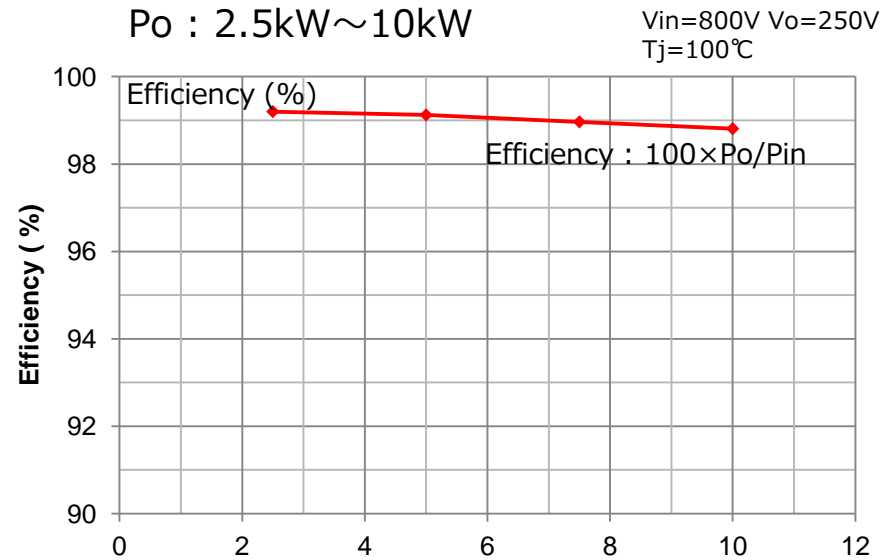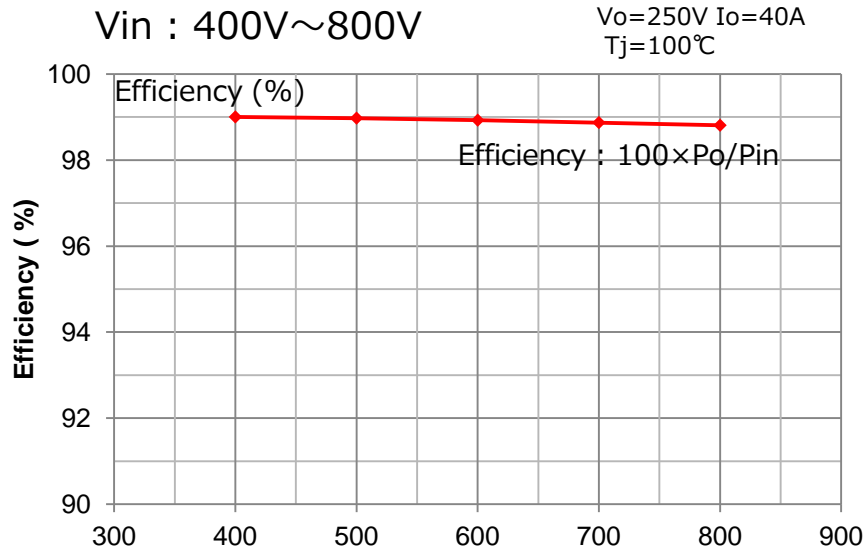

Efficiency, Power Dissipation 2

