## BD7693FJ-EVK-001 Parts list



Item	Specifications	Parts name	Manufacture
C1,C2,C3	470 n, 310 Vac	890334025039CS	WURTH ELECTRONIK
C4,C15	0.1 uF, 630 Vdc	890303425004CS	WURTH ELECTRONIK
C5	220 u, 450 V	LGN2W221MELA40	NICHICON
C6,C8,C9,C12,C19,D2,R4,R8,R16,R18,ZNR1	NON MOUNTED		
C7	0.68 μF, 50 V	885012206051_	WURTH ELECTRONIK
C10	100 pF, 100 V	HMK107SD101KA-T	TAIYO YUDEN
C11	220 pF, 2k V	885342209008	WURTH ELECTRONIK
C13,C14	2200 pF, 300 V	DE1E3RA222MJ4BP01F	MURATA
C16	0.01 μF, 50 V	885012206089_	WURTH ELECTRONIK
C18	33 μF, 50 V	86020672012_	WURTH ELECTRONIK
DA1	600 V, 15 A	GBU15J-U1	WILLAS Corp.
D1	FRD,10 A, 600 V	RFNL10TJ6S	ROHM
D3	15A , 600 V	RFNL15TJ6S	ROHM
D4,D6	FRD, 0.5 A, 200 V	RF05VAM2S	ROHM
F1	250 Vac, 6.3 A	VBS UDA-A6.30A	TAN DOE Corp.
IC1	·	BD7693FJ	ROHM
Q1	600 V, 24 A	R6024KNX	ROHM
R1	820 kΩ	KTR18EZPF8203	ROHM
R2	750 kΩ	KTR18EZPF7503	ROHM
R3	10 kΩ	MCR03EZPFX1002	ROHM
R5,R6	680 kΩ	KTR18EZPJ684	ROHM
R7	6.8 kΩ	MCR03EZPJ682	ROHM
R10	100 Ω	MCR18EZPJ101	ROHM
R11	10 Ω	MCR18EZPJ100	ROHM
R12	220 Ω	MCR18EZPJ221	ROHM
R13	15 kΩ	MCR18EZPJ153	ROHM
R14,R15	220 mΩ	LTR50EZPZFLR220	ROHM
R17	10 Ω	ERG2SJ100V	PANASONIC
TH1	2 Ω, 4 Α	2D2-13LD	SEMITEC
R20,R21,R22	130 kΩ	MCR18EZPJ134	ROHM
R23,R24	100 kΩ	MCR18EZPJ104	ROHM
R25	22 kΩ	MCR18EZPJ223	ROHM
FL1	35 mH / 3.5 A	7748040435	WURTH ELECTRONIK
FL2	15 mH	GSTC1810-153N	GANG SONG
HEAT1,HEAT3	11.5 K/W	30PBE30-30B	MARUSAN ELECTRONICS
HEAT2	22.9 k/W	IC-1625-STL	SANKYO THRMOTECH
CN1	3pin	B03P – NV(LF)(SN)	JST
CN2	3pin	691137910003_	WURTH ELECTRONIK
L1	230 µH 7.4A	PFC3819QM-231K07D-50	TDK
L2	90 μH	7447013	WURTH ELECTRONIK
L3	10 μH	744750420100	WURTH ELECTRONIK
	το μιτ	/ ++/30+20100_	TTORTH ELLCTRONIK

## Important Notes on the Use of Reference Designs

- 1) The contents of this document are subject to change without notice for the purpose of improvement.
- 2) ROHM provides reference designs (including, but not limited to, circuit diagrams, layout data, parts lists, reference boards and their evaluation results, etc.) and all materials related to evaluation boards (hereinafter collectively referred to as "Reference Designs, etc.") to customers for the purpose of referencing them in the development of devices, equipment, software, etc. incorporating ROHM products (hereinafter collectively referred to as "Customer Products"). The design, verification, etc. required for the development of the Customer's Product shall be done at the customer's responsibility and expense. In no event shall the customer use the Reference Designs, etc. for any purpose other than the purpose mentioned above.
- 3) Reference Designs, etc. are provided on an "as is" basis. ROHM disclaims all warranties, express or implied, including, but not limited to, warranties of usefulness, functionality, accuracy, merchantability, and fitness for a particular purpose. In no event shall ROHM be liable for any damages (including, but not limited to, lost profits or other incidental, consequential, or punitive damages) arising out of, related to or in connection with the use of or application of the Reference Designs, etc. whether in contract or tort. For the avoidance of doubt, ROHM does not warrant that the Reference Designs, etc. will work with the Customer's Product.
- 4) When using Reference Designs, etc. be sure to request and verify the latest specifications (including the specifications of the products that compose the Reference Design, etc.) separately.
- 5) The customer shall be responsible for implementing safety measures such as derating, redundant design, fire prevention, backup, and fail-safe measures, etc., to prevent personal injury, fire damage, etc., caused by the Customer's Product developed with Reference Designs, etc. ROHM assumes no liability whatsoever for any use in excess of the ratings or in case of failure to observe the instructions for use.
- 6) The application circuit examples, constants, and other information provided in Reference Designs, etc. are intended to illustrate standard operation and usage. Therefore, when designing for mass production, please take into account various external conditions.
- 7) Reference Designs, etc. are intended to show typical operations and examples of application circuits, etc., and do not constitute a license, express or implied, to implement or use any intellectual property rights or any other rights of ROHM or any other company. ROHM shall not be liable for any disputes arising from, related to or in connection with the use of the Reference Designs, etc.
- 8) Please make sure to contact ROHM and obtain ROHM's consent before using the Reference Designs, etc. for the following Customer's Product that requires particularly high reliability. Transportation equipment (in-vehicle, ship, railroad, etc.), trunk line communication equipment, traffic signal equipment, disaster and security equipment, safety equipment, medical equipment, servers, solar cells, power transmission systems, etc.
- 9) Do not use Reference Designs, etc. for the following Customer's Product that requires extremely high reliability. Aerospace equipment, nuclear power control equipment, submarine relay equipment, etc.
- 10) Do not use Reference Designs, etc. for military use, such as development of weapons of mass destruction, or for any other military purpose.
- 11) ROHM does not assume any liability for any accidents or damages caused by non- compliance with the descriptions in this document.
- 12) The information contained in this document has been carefully prepared to ensure accuracy. However, ROHM shall not be liable for any loss or damage incurred by customers due to errors or misprints in this document.
- 13) Do not reproduce or duplicate any part of this document in any form or by any means without ROHM's permission.



Thank you for your accessing to ROHM product informations. More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

http://www.rohm.com/contact/

R2109A www.rohm.com