

LogiCoA001-EVK-001 Parts List



Quantity	Reference Designator	Part Number	Manufacturer	Value	Description [Unit: inch(mm)]
<b>IC</b>					
1	IC1	BD2320EFJ-LAE2	ROHM	-	Gate Driver,14.5V,2024(4960)
1	IC2	BD950N1WG-CTR	ROHM	-	LDO, 42V, 5V/150mA,1112(2829)
1	IC3	ML62Q2035-NNNTDZWATZ	LAPIS Technology	-	MCU, 5.5V, 32kbyte,2526(6465)
1	IC4	BD900N1WG-CTR	ROHM	-	LDO, 42V, 150mA,1112(2829)
1	U1	BU7481SG-TR	ROHM	-	1ch-OPAMP,5.5V,1112(2829)
<b>Resistor</b>					
1	R1	-	-	4.7Ω	0.1W,±1%,0603(1608)
3	R2,R22,R42	-	-	0Ω	1A,0.1W,0603(1608)
4	R3,R4,R12,R14	-	-	10kΩ	0.1W,±1%,0603(1608)
1	R5	LTR100LJZPFSR020	ROHM	20mΩ	4W,±1%,1225(3264)
1	R6	-	-	220kΩ	0.1W,±1%,0603(1608)
1	R7	-	-	27kΩ	0.1W,±1%,0603(1608)
6	R8,R13,R15,R19,R31,R33	-	-	2.2kΩ	0.1W,±1%,0603(1608)
1	R9	-	-	330Ω	0.1W,±1%,0603(1608)
1	R10	-	-	820Ω	0.1W,±1%,0603(1608)
1	R11	-	-	150Ω	0.1W,±1%,0603(1608)
4	R16,R17,R32,R44	-	-	4.7kΩ	0.1W,±1%,0603(1608)
3	R18,R35,R36	-	-	100Ω	0.1W,±1%,0603(1608)
1	R20	-	-	470Ω	0.1W,±1%,0603(1608)
2	R21,R24	-	-	1kΩ	0.1W,±1%,0603(1608)
0	R23	No mount	-	-	-
1	R25	-	-	8.2kΩ	0.1W,±1%,0603(1608)
4	R26,R27,R38,R40	-	-	10Ω	0.1W,±1%,0603(1608)
1	R28	-	-	43Ω	0.1W,±1%,0603(1608)
1	R29	-	-	51Ω	0.1W,±1%,0603(1608)
1	R30	-	-	3.3kΩ	0.1W,±1%,0603(1608)
0	R39,R41	No mount	-	-	-
1	R43	-	-	82kΩ	0.1W,±0.5%,0603(1608)
1	R44	-	-	4.7kΩ	0.1W,±0.5%,0603(1608)
1	VR1	CT-6EP103	Nidec Copal Electronics	10kΩ	70.7V,0.5W,±10%,2828(7070)
<b>Capacitor</b>					
4	C1,C2,C3,C4	C3225X7S2A475K200AE	TDK	4.7μF	100V,X7S,±10%,1210(3225)
4	C5,C19,C24,C25	CGA3E1X7R1E105K080AC	TDK	1μF	25V,X7R,±10%,0603(1608)
3	C6,C18,C31	CGA3E2X7R1H104K080AA	TDK	0.1μF	50V,X7R,±10%,0603(1608)
6	C7,C8,C9,C10,C11,C12	GRM32ER71E226ME15L	Murata	22μF	25V,X7R,±20%,1210(3225)
2	C13,C35	GRM21BR61H475ME51L	Murata	4.7μF	50V,X5R,±20%,0805(2012)
2	C14,C36	GRM188R6YA475ME15D	Murata	4.7μF	35V,X5R,±20%,0603(1608)
2	C15,C22	CC0603JRNPO9BN470	Yageo	47pF	50V,COG,±5%,0603(1608)
0	C16	No mount	-	-	-
2	C17,C21	GRM188B11H103K	Murata	0.01μF	50V,B,±10%,0603(1608)
1	C20	CGA3E2C0G1H471J080AA	TDK	470pF	50V,COG,±5%,0603(1608)
1	C23	CGA3E3X7R1H224K080AB	TDK	0.22μF	50V,X7R,±10%,0603(1608)
2	C26,C33	CGA3E2X7R1H102K080AA	TDK	1000pF	50V,X7R,±10%,0603(1608)
1	C27	CGA3E2C0G1H822J080AA	TDK	8200pF	50V,COG,±5%,0603(1608)
1	C28	CGA3E2C0G1H561J080AA	TDK	560pF	50V,COG,±5%,0603(1608)
2	C29,C30	CGA3E2C0G1H101J080AA	TDK	100pF	50V,COG,±5%,0603(1608)
1	C32	CGA3E2X7R1H223M080AA	TDK	0.022μF	50V,X7R,±15%,0603(1608)
1	C34	C1608X5R1E475M080AC	TDK	4.7μF	25V,X5R,±20%,0603(1608)
1	CE1	UCDH101MCL6GS	Nichicon	100μF	50V,±20%,0.36Ωmax,Φ10
1	CE2	APXT100ARA391MF80G	Chemicon	390μF	10V,±20%,22mΩmax,Φ6.3
<b>Diode</b>					
1	D1	RB510SM-40T2R	ROHM	-	40V,100mA,0603(1608)
1	D2	RB500SM-30T2R	ROHM	-	30V,100mA,0603(1608)
1	D3	1SS355VMTE-17	ROHM	-	80V,100mA,1005(2513)
2	ZD1,ZD2	EDZVT2R6.2B	ROHM	-	6.2V,5mA,150mW, 0603(1608)
<b>Transistor</b>					
1	TR1	2SA2029T2LR	ROHM	-	-50V,150mA,0505(1211)
2	FET1,FET2	RS6L090BGTB1	ROHM	-	60V,90A,4.7mΩmax,2024(4960)
<b>Inductor</b>					
1	L1	XAL1010-153MED	Coilcraft	15μH	60V,9.9A,18.6mΩmax,±20%,(10.0 x 11.3)
<b>LED</b>					
1	LED1	SML-D13U8WT86	ROHM	-	RED,2.1V,20mA,52mW,0603(1608)
1	LED2	SML-D12P8WT86	ROHM	-	GRN,2.2V,20mA,54mW,0603(1608)
<b>Others</b>					
1	J3	HIF3FC-14PA-2.54DSA(71)	Hirose Electric	-	200V,1A,IMD14-2.54-H9.3-
2	JP_LDO,JP_12V	61300211121	Würth Elektronik	-	250V,3A,2.54,5.08*2.54
2	JP_Loop,JP_REG	61300311121	Würth Elektronik	-	250V,3A,2.54,7.62*2.54
1	SW_RC	ATE1E-2M3-10-Z	Nidec Copal Electronics	-	ON-OFF-ON,2.54-ATE1,60V,50mA,0.4VA
2	J1,J2	XW4E-02C1-V1	Omron	-	250V,13.5A,5.08-XW4E,250V,13.5A
1	FT234x	AE-FT234X	AKIZUKI DENSHI TUSHO	-	5V, 2.54, FT234XD

## Important Notes on the Use of Reference Designs

- 1) The contents of this document are subject to change without notice for the purpose of improvement.
- 2) ROHM provides reference designs (including, but not limited to, circuit diagrams, layout data, parts lists, reference boards and their evaluation results, etc.) and all materials related to evaluation boards (hereinafter collectively referred to as "Reference Designs, etc.") to customers for the purpose of referencing them in the development of devices, equipment, software, etc. incorporating ROHM products (hereinafter collectively referred to as "Customer Products"). The design, verification, etc. required for the development of the Customer's Product shall be done at the customer's responsibility and expense. In no event shall the customer use the Reference Designs, etc. for any purpose other than the purpose mentioned above.
- 3) Reference Designs, etc. are provided on an "as is" basis. ROHM disclaims all warranties, express or implied, including, but not limited to, warranties of usefulness, functionality, accuracy, merchantability, and fitness for a particular purpose. In no event shall ROHM be liable for any damages (including, but not limited to, lost profits or other incidental, consequential, or punitive damages) arising out of, related to or in connection with the use of or application of the Reference Designs, etc. whether in contract or tort. For the avoidance of doubt, ROHM does not warrant that the Reference Designs, etc. will work with the Customer's Product.
- 4) When using Reference Designs, etc. be sure to request and verify the latest specifications (including the specifications of the products that compose the Reference Design, etc.) separately.
- 5) The customer shall be responsible for implementing safety measures such as derating, redundant design, fire prevention, backup, and fail-safe measures, etc., to prevent personal injury, fire damage, etc., caused by the Customer's Product developed with Reference Designs, etc. ROHM assumes no liability whatsoever for any use in excess of the ratings or in case of failure to observe the instructions for use.
- 6) The application circuit examples, constants, and other information provided in Reference Designs, etc. are intended to illustrate standard operation and usage. Therefore, when designing for mass production, please take into account various external conditions.
- 7) Reference Designs, etc. are intended to show typical operations and examples of application circuits, etc., and do not constitute a license, express or implied, to implement or use any intellectual property rights or any other rights of ROHM or any other company. ROHM shall not be liable for any disputes arising from, related to or in connection with the use of the Reference Designs, etc.
- 8) Please make sure to contact ROHM and obtain ROHM's consent before using the Reference Designs, etc. for the following Customer's Product that requires particularly high reliability. Transportation equipment (in-vehicle, ship, railroad, etc.), trunk line communication equipment, traffic signal equipment, disaster and security equipment, safety equipment, medical equipment, servers, solar cells, power transmission systems, etc.
- 9) Do not use Reference Designs, etc. for the following Customer's Product that requires extremely high reliability. Aerospace equipment, nuclear power control equipment, submarine relay equipment, etc.
- 10) Do not use Reference Designs, etc. for military use, such as development of weapons of mass destruction, or for any other military purpose.
- 11) ROHM does not assume any liability for any accidents or damages caused by non-compliance with the descriptions in this document.
- 12) The information contained in this document has been carefully prepared to ensure accuracy. However, ROHM shall not be liable for any loss or damage incurred by customers due to errors or misprints in this document.
- 13) Do not reproduce or duplicate any part of this document in any form or by any means without ROHM's permission.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

### ROHM Customer Support System

<http://www.rohm.com/contact/>